


# 7.2. Gekoppelte Schwingkreise



Induktive Kopplung:

$$L_1 \ddot{Q}_1 + R_1 \dot{Q}_1 + \frac{1}{C_1} Q_1 = -L_{12} \ddot{Q}_2$$
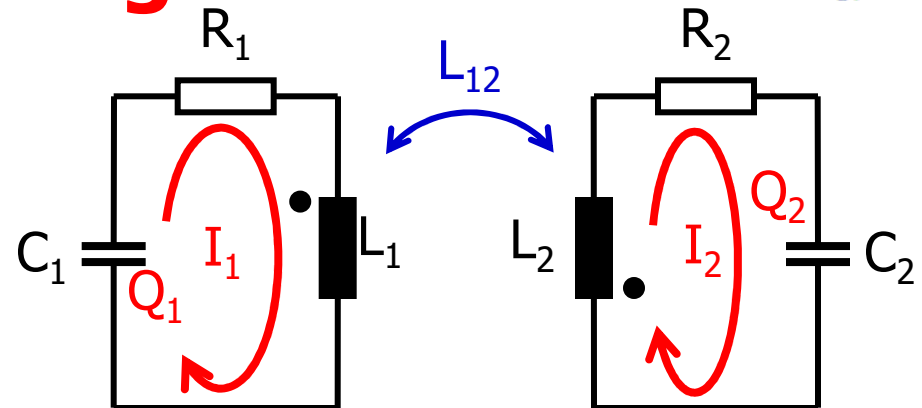
$$L_2 \ddot{Q}_2 + R_2 \dot{Q}_2 + \frac{1}{C_2} Q_2 = -L_{12} \ddot{Q}_1$$



Lösungsweg: Transformation auf **Normalkoordinaten**

Beispiel:  $L_1 = L_2 = L$      $C_1 = C_2 = C$      $R_1 = R_2 = R$

**Normalkoordinaten:**  $Q_{\pm} = Q_1 \pm Q_2$      $(L \pm L_{12}) \ddot{Q}_{\pm} + R \dot{Q}_{\pm} + \frac{1}{C} Q_{\pm} = 0$


**Eigenfrequenzen:**  $\omega_{\pm} = \sqrt{\frac{1}{(L \pm L_{12})C} - \frac{1}{4} \alpha_{\pm}^2}$      $\alpha_{\pm} = \frac{R}{L \pm L_{12}}$

**Normalmoden ( Schwingfall ):**  $Q_{\pm} \sim e^{-\frac{1}{2} \alpha_{\pm} t} e^{i \omega_{\pm} t}$


# Andere (analoge) Kopplungen



Kapazitive Kopplung:


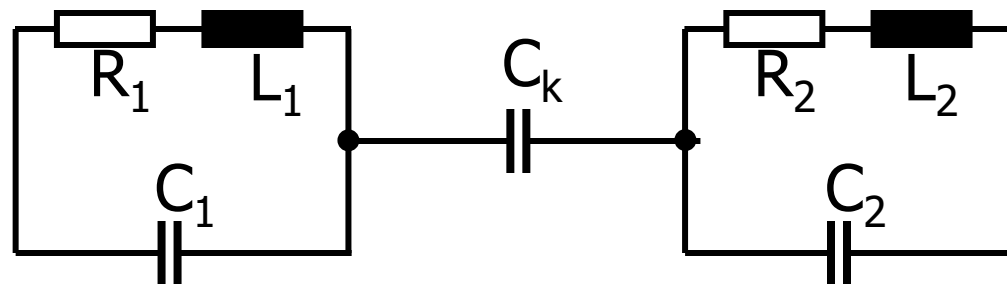


Galvanische Kopplung:

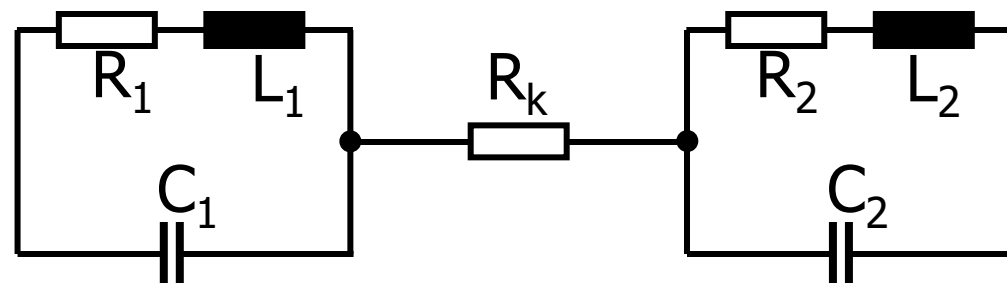

# 7. 3. Ungedämpfte Schwingungen

Beispiel: **Meißner-Schaltung**

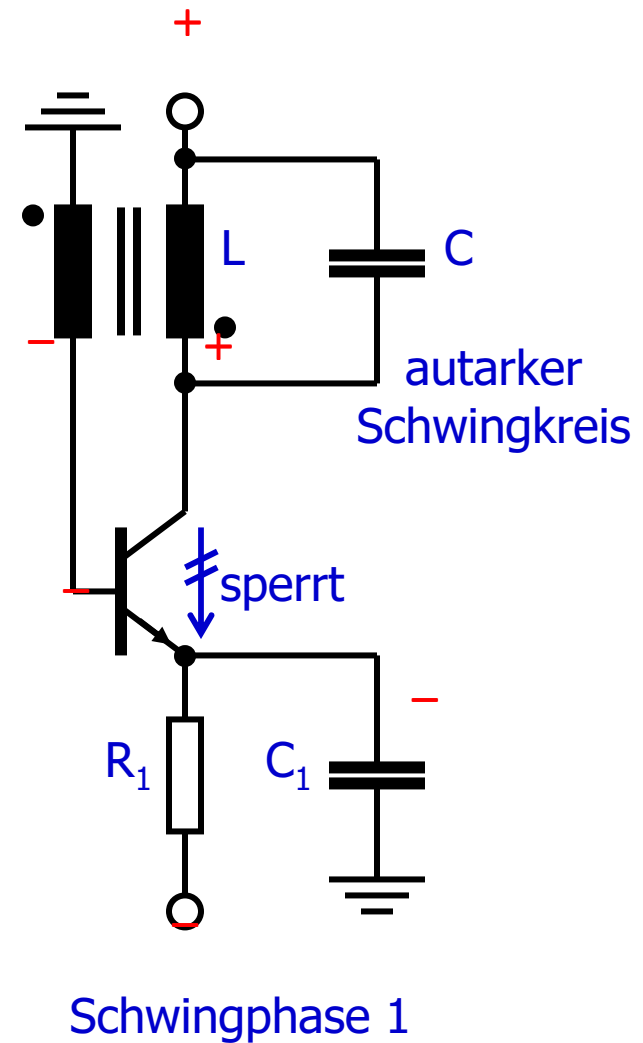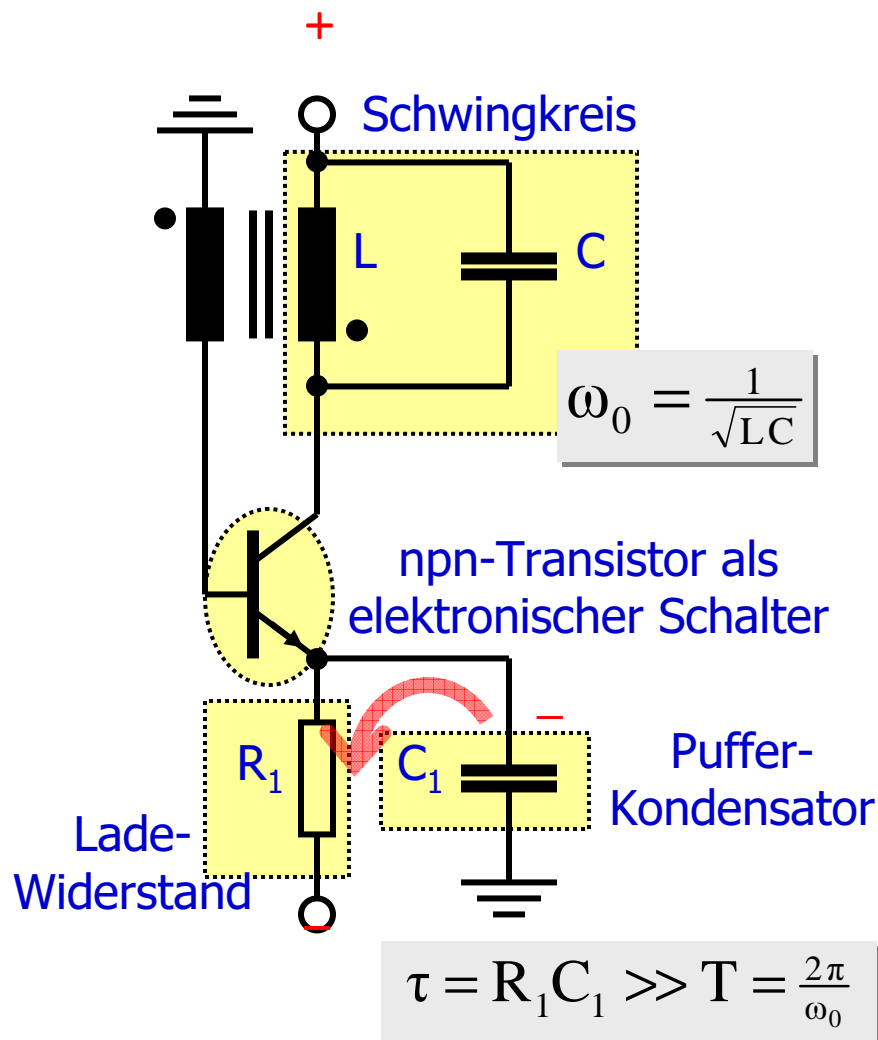

# Meißner-Schaltung

